

**EXCLUSIVE!**

**Popular Electronics®**  
NOVEMBER, 1975

# The First Motorola/AMI '6800' MPU Computer Project



*Features compact size, simplified construction,  
built-in TTY interface, and low cost.*

**BY H. EDWARD ROBERTS & PAUL VAN BAALEN**


**L**ARGE-SCALE integration (LSI) has provided many useful IC chips for the hobbyist. One of the latest LSI devices is the microprocessor unit (MPU), which has made it possible to build microcomputers that are fairly easy to assemble at moderate cost. The most popular MPU's are the 8008 and 8080 due to their reasonable cost and wide availability in computer kits.


However, many knowledgeable hobbyists have been looking for a microcomputer built around one of a number of other MPU's available (just as some people would like to try a diesel or steam engine to replace the gasoline motor). Most of these readers have told us they were interested in the Motorola M6800 MPU (for one reason or another). Many also felt that the price of a microcomputer was still too high. POPULAR ELECTRONICS is therefore pleased to introduce the first microcomputer using the 6800 MPU in a design that substantially reduces cost.

**T**HE Altair 680 is a complete microcomputer built around the 6800 MPU available from Motorola and American Micro-Systems, Inc. Measuring a very compact 11 1/16"W x 11 1/16"D x 4 11/16"H (28.1 x 28.1 x 11.9 cm), the 680 is less than one-third the size of the Altair 8800. Although both computers have MPU's with the same memory capacity, the 680's smaller enclosure makes internal expandability significantly less. However, it is more than adequate for most applications. More importantly, the 680 costs less than half the price of the 8800 when the two machines are configured similarly in a minimum system

Other attributes of the new computer include ease of assembly (only one large pc board), built-in TTY interface, and high speed (4- $\mu$ s minimum cycle time). The last is some 10 to 50 times faster than earlier small computers built around the 8008 MPU but half the speed of the 8800.

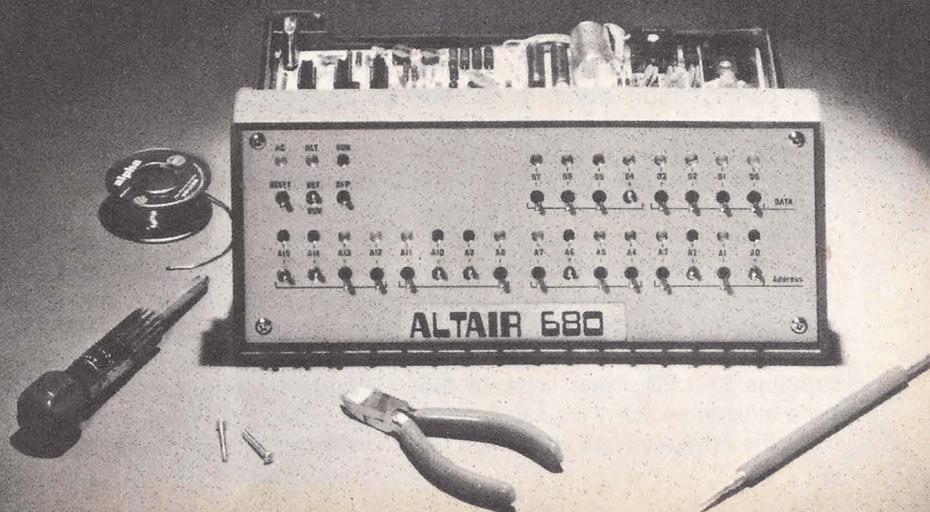Another meaningful consideration in a 6800-MPU computer design is the raft of instructional material readily available from Motorola Semiconductor Products, Inc., including the "M6800 Microprocessor Programming Manual." Too, the 6800 is TTL compatible and uses just one 5-volt power supply.



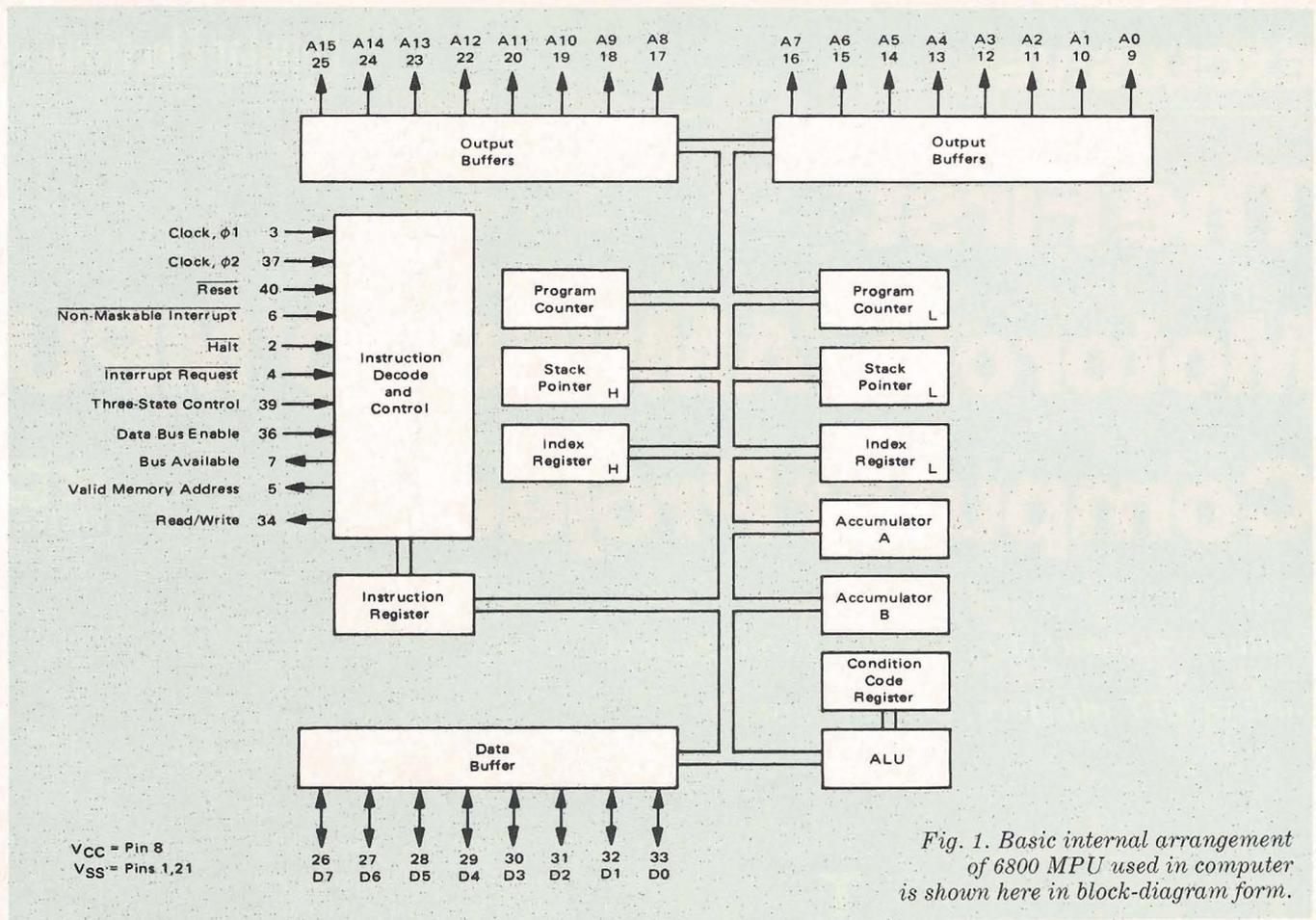

**Basic System Philosophy.** The basic MPU, memory, I/O (input/output), and power-supply circuits in the Altair 680 are located on a single printed circuit board. The addition of a compact power transformer makes this assembly a complete computer system. (Front-panel switch programming can be used, but in the absence of this assembly, PROM's or ROM's must be installed for programming.)

The front-panel assembly contains all the logic needed to reset, halt, or start the processor. Also, any memory cell can be read or written into from the front panel via 16 ADDRESS and eight DATA switches. Mounted on the front-panel circuit board is a 100-contact edge connector that permits the main MPU board to plug directly into the front panel, thus eliminating the need for a wiring harness. (In systems that do not use the front-panel assembly, the MPU board automatically starts running at an address specified by either a PROM or a hard-wired patch.) The front panel contains 27 LED's that indicate the state of each switch. As a safety measure, the POWER switch is located on

the back of the cabinet to obviate the possibility of its being accidentally operated during programming.

The basic computer contains 1024 bytes of memory and has provisions for an additional 1024 bytes of PROM or ROM memory. An I/O channel and interface are also included in the basic system. The I/O channel can be configured to interface RS-232 or a 20-mA or 60-mA TTY loop. This means that anyone who can obtain an old five-level Baudot-type Teletype—such as the MOD-15, MOD-19, etc.—can use it as a computer terminal. (Many such Teletypes are available for less than \$100 and frequently for as little as \$25 nationwide.)

The Altair 680 can be built with either a full-programmability or a "turn-key" front panel. The latter eliminates all controls except restarting the processor. There are a number of applications where this is desirable to eliminate the possibility of having an operator affect the contents of the memory or the computing cycle. An example might be in a sophisticated intruder-detection system where the only control provided for the operator is essentially on/off.

**Software.** The software associated with the 6800 MPU includes an editor, PROM monitor, and assembler, as contrasted to the editor, assembler, monitor and basic for the Altair 8800 computer.

**System Details.** The Altair 680 computer is composed of five sections: MPU and clock, memory, control and indication, I/O port, and power supply.

**MPU and Clock.** As mentioned earlier, the MPU and clock are the new 6800 LSI chip. Its basic internal arrangement is shown in Fig. 1. The main elements are instruction decode and control, instruction register, data and address registers and buffers, 16-bit index register, 16-bit program counter, 16-bit stack pointer, two 8-bit accumulators, condition code register, and ALU (arithmetic logic unit).


The timing and control inputs and outputs for the 6800 chip are:

Phase 1 and phase 2 clock ( $\phi 1, \phi 2$ )—a nonoverlapping 500-kHz clock at  $V_{cc}$ .

Address bus A0 through A15—16 high active outputs that determine address or I/O sections to use.
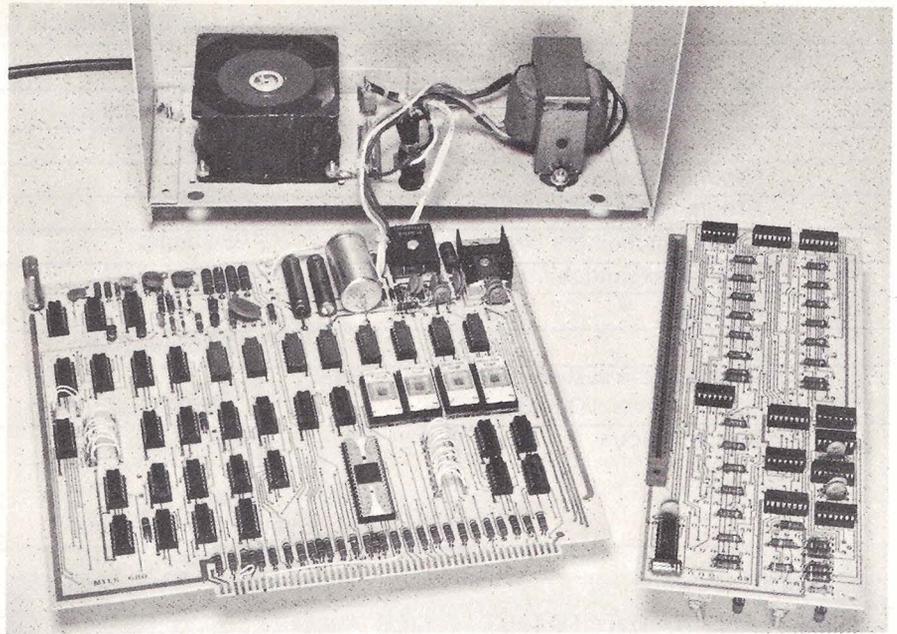
## DISPLAY PARTS LIST

C1, C4—0.33- $\mu$ F, 12-V disc ceramic capacitor  
 C2, C3—0.47- $\mu$ F, 12-V disc ceramic capacitor  
 DA00 to DA15, DD00 to DD07, and DS1 to DS3—RL21 light-emitting diode  
 ICA, ICB, ICC, ICD, ICE, ICF, ICG, ICH—74LS05  
 ICE, ICF, ICG, ICH—4449  
 ICJ—74L00  
 ICK, ICL—26L123  
 Following resistors are 1/2-watt, 5%:  
 R1 to R16, R20 to R27—1500 ohms  
 R17 to R19—20,000 ohms  
 R28 to R30, R33 to R37—4700 ohms  
 R31 to R38—1000 ohms  
 R39, R40—10,000 ohms  
 SC1 to SC12—0.1- $\mu$ F, 12-V disc ceramic capacitor  
 SA00 to SA15, SD00 to SD07, S24—Spdt toggle switch  
 S26, S27—Spdt momentary toggle switch  
 Misc.—100-contact edge connector



Almost entire computer is assembled on a single large pc board (left). Board at right is for front panel. Boards plug together.

Data bus D0 through D7—eight high active bidirectional lines for transfer to and from memory and peripherals.

Halt signal ( $\overline{\text{HLT}}$ )—low active input that ceases activity in the computer.

Read/write signal (R/W)—in the high state, signals the memory and peripherals that the MPU is in the read condition; in the low state, signals that the MPU is in the write condition.

Valid memory address (VMA)—signals external devices (memory and I/O) that the MPU has a valid address on the memory bus.

Data bus enable (DBE)—enables the bus drivers.

Bus available (BA)—indicates machine has stopped and address bus is available.

Reset ( $\overline{\text{RES}}$ )—resets and starts the MPU from a power-off condition. A positive-going edge on this input tells the MPU to begin the restart sequence.

Interrupt request ( $\overline{\text{IRQ}}$ )—when low, tells the MPU to start an interrupt sequence (save the registers on the stack, set interrupt mask bit high so no other interrupts can occur, and vector to the interrupt address). This type of interrupt can only occur if the interrupt mask bit in the condition code register is low.

Nonmaskable interrupt ( $\overline{\text{NMI}}$ )—

essentially the same as the  $\overline{\text{IRQ}}$ , except it is not dependent on the condition code register.

The clock is a 2-MHz crystal-controlled oscillator that uses a pair of inverters that drive flip-flops to form a 500-kHz, two-phase clock that is distributed to the MPU, memory, and I/O sections in the computer via inverters and buffers.

**Memory.** The memory system consists of 1024 words of 8-bit-wide RAM, using 2102-type 1024  $\times$  1-bit devices, and up to 1024 words of PROM, using ultraviolet-erasable 1702 devices. The basic arrangement is shown in Fig. 2. The low-order address bits are fed to both the RAM's and PROM's.

**Front Panel.** The front panel assembly contains the RUN/HALT switch, with a LED for each switch position; a reset switch with no LED indicator; and the ac power ON LED indicator (Fig. 3). The 16 ADDRESS switches and eight DATA switches each have their own LED indicator.

The DEPOSIT, RESET, DATA, and ADDRESS switches are enabled only when the RUN/HALT switch is in the HALT position, at which time, a retriggerable one-shot multivibrator drives the halt input of the MPU low. This, in turn, drives the bus-available (BA) signal high and also conditions the other switches. To view the data in any memory location, the RUN/HALT switch must be placed in the HALT position and the ADDRESS switches set to the required address. The data at that

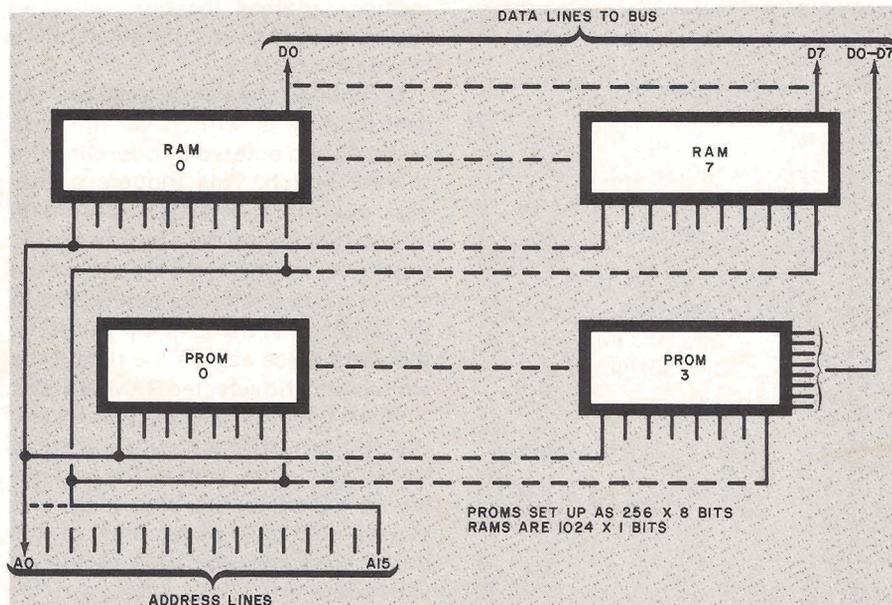


Fig. 2. There are eight RAM's (RAM 0 through RAM 7) and four PROM's (PROM 0 through PROM 3) in the computer's memory system.

## ALTAIR COMPUTER COMPARISON CHART

Features	Altair 680	Altair 8800
Maximum word size	24 bits (byte oriented)	24 bits (byte oriented)
Arithmetic unit	8-bit parallel	8-bit parallel
Minimum cycle time	4 $\mu$ s	2 $\mu$ s
Program instructions	72	78
Maximum memory size	65k bytes	65k bytes
Internal expandability	5 interface cards	250 interface cards
Interrupt	3 levels	8 levels
MPU	6800 (Motorola, AMI)	8080 (Intel, TI)
Approximate system cost (1k memory, I/O, case, P/S)	\$300	\$600
Miscellaneous	Fewer parts 2 printed circuit boards Smaller size Built-in TTY interface	Minimum of 4 pc boards

### MAIN BOARD PARTS LIST

BD1—Bridge rectifier (VJ048)  
 C1—3300- $\mu$ F, 50-V electrolytic capacitor  
 C2, C3—100- $\mu$ F, 50-V electrolytic capacitor  
 C4 to C9—0.33- $\mu$ F, 50-V disc ceramic capacitor  
 C10, C13—0.1- $\mu$ F, 16-V disc capacitor  
 C11, C12—0.33- $\mu$ F, 16-V disc capacitor  
 C14—0.01- $\mu$ F, 16-V disc capacitor  
 C15—1- $\mu$ F, 50-V electrolytic capacitor  
 D1, D2, D7 to D12—1N4004 diode  
 D3 to D6—1N4739A, 9.1-V zener diode  
 F1—1-A, 250-V ac, 3-AG fuse  
 ICA—7404  
 ICB—7473  
 ICC, ICUU—7408  
 ICD, ICE, ICS—4449  
 ICF, ICG—74LS01  
 ICH, ICJ, ICK, ICL, ICM, ICN, ICP, ICR—2102  
 ICT, ICU, ICGG, ICHH, ICPP, ICRR—74LS30

ICV—74L00  
 ICW—74L74  
 ICX, ICY, ICTT—4050  
 ICZ, ICAA, ICBB, ICCA—1702  
 ICDD, ICFF—74L04  
 ICEE, ICMM—74L10  
 ICJJ—6800  
 ICKK, ICLL, ICSS—74LS05  
 ICNN—74LS27  
 Q1, Q3, Q4—TIS98  
 Q2—EN3907

Except where noted, following resistors are  $\frac{1}{2}$ -watt, 5%:

R1, R2—33 ohms, 2-watt, 5%  
 R3, R4, R5, R7—100 ohms  
 R6—130 ohms, 1-watt, 5%  
 R8, R11—800 ohms  
 R9—220 ohms, 1-watt, 5%  
 R10, R28 to R51—7500 ohms  
 R12, R15, R16, R17—1000 ohms  
 R13—470 ohms  
 R14, R20, R21—390 ohms  
 R18, R19—330 ohms  
 R22—33,000 ohms  
 R23, R24, R25, R60—10,000 ohms

R26, R27, R56, R57, R58, R59—not used  
 R52 to R55—3000 ohms  
 SP1—Spdt toggle switch  
 T1—5-volt, 1.2-A transformer  
 VR1—7805 regulator  
 XTAL—2-MHz crystal

Misc.—Fuse holder (Buss HKP-CC, line cord, fan (IMC 3 $\frac{3}{8}$ "), I/O socket (DB-255), sockets (14-pin, 22; 16-pin, 20; 24-pin, 4; 40-pin, 1), case optional).

Note—The following are available from MITS, 6328 Linn, N.E., Albuquerque, NM 87108: complete kit (all parts) #680F at \$293; complete kit except for front panel board #680T at \$240; kit #680MPU, including pc board, 6800 MPU, 1k memory, and all main board components except power supply at \$180; front panel and MPU pc boards #680PC at \$48; I/O socket kit at \$29; fan kit at \$16; 256 x 8-bit PROM kit at \$42; construction information package is free, with self-addressed stamped 9" x 12" envelope.

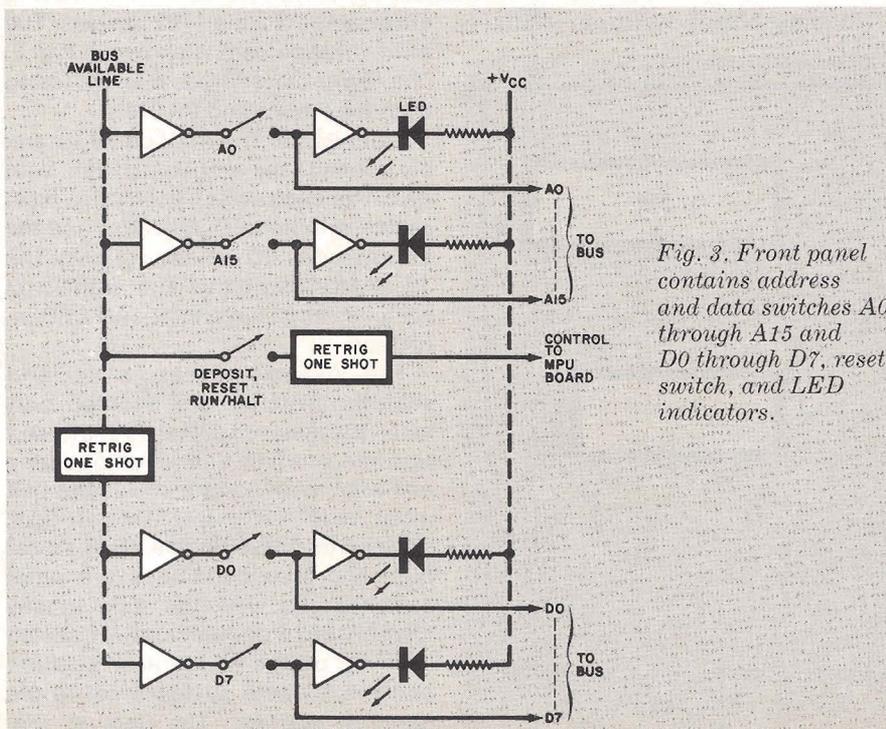


Fig. 3. Front panel contains address and data switches A0 through A15 and D0 through D7, reset switch, and LED indicators.

memory address location will then appear as lighted and unlighted LED's in the DATA display.

To change data in a location, the desired data is written via the DATA switches and entered by operating the DEPOSIT switch. This triggers a one-shot multivibrator, enabling the data information to the data bus and causing the R/W signal to go low. Since the address bus is already connected to the switches by being in the halt state, the write pulse causes the data to be written into the selected RAM address.

When the RESET switch is operated, the CPU resets. This, in turn, initiates a restart sequence. That is, the address bus is pulled to the high state and causes the hard-wired data in the board jumpers to be used as the restart address.

Access to the I/O port is gained by addressing location 17577 (in octal). A sequence of events then occurs that

causes an output to the built-in TTY output jack and at the Teletype itself.

**Power Supply.** The main 5-volt line is generated within the computer by a conventional bridge rectifier, filter capacitor, and IC regulator circuit. A 32-volt winding on the transformer is used to generate the unregulated  $\pm 16$  volts required for the TTY interface system, while a  $-16$ -volt line is fed to

four zener-diode-regulated outputs to provide four 9-volt lines for the PROM's.

**Construction.** The actual-size etching and drilling guides for the computer boards are larger than our page size. Rather than reducing or cutting them up to fit our pages, a free construction package is available. If you

wish to obtain a construction information package, simply send a self-addressed stamped 9" x 12" envelope to the address given at the end of the Parts List.

The construction package contains full-size schematics, full-size etching and drilling guides, component-placement diagrams, and front-panel layout. ◆

## CRAMER ELECTRONICS ENTERS OEM COMPUTER KIT MARKET

**T**HE major reason for the tremendous success of the various computer kits on the market is that they save considerable time. One doesn't have to hunt down the MPU's, memories, etc., that must be accumulated before embarking on a home computer project. It appears that OEM engineers are also spending considerable time in hunting down computer parts. Cramer Electronics, one of the leading U.S. electronic parts distributors, has decided to enter the computer kit business, with emphasis on the OEM market.

Cramer is starting with three kits, separately based on the Intel 8080, Motorola 6800, and Texas Instruments TMS8080 MPU's. Each of the kits

shares a common \$495 price tag.

You get a lot for \$495: complete color-coded schematic diagram; RAM with 1024 (8-bit) bytes, expandable to 65 k bytes; erasable PROM with 1024 (8-bit) bytes; support circuitry, including clock, complete buffering, control and synchronization logic, interrupts, DMA controls; etc. The PROM gives you a program to run at the outset. There are at least four 8-bit-wide input and output ports, with expandability to 512 ports, decoding for 16 of which is included.


The PROM contains a system monitor to permit the computer to be used as soon as it is assembled. Programs can be entered, modified, examined, and executed under switch

control or by typed-in commands. A cassette program, included with the kit, can be used to debug the computer. Finally, a complete user manual gives hints on programming and how to expand the computer.

All together, there are about 190 parts in each kit, adding up to a total catalog value of some \$700. Software is included in the kits to help in programming via front-panel switches and LED's, cassette tape, Teletypewriter, or any RS-232-compatible terminal. Not supplied are printed circuit boards, power supply, and cabinet.

For more information about the new computer kits, write to: Cramer Electronics, Inc., 65 Wells Ave., Newton, MA 02159. ◆
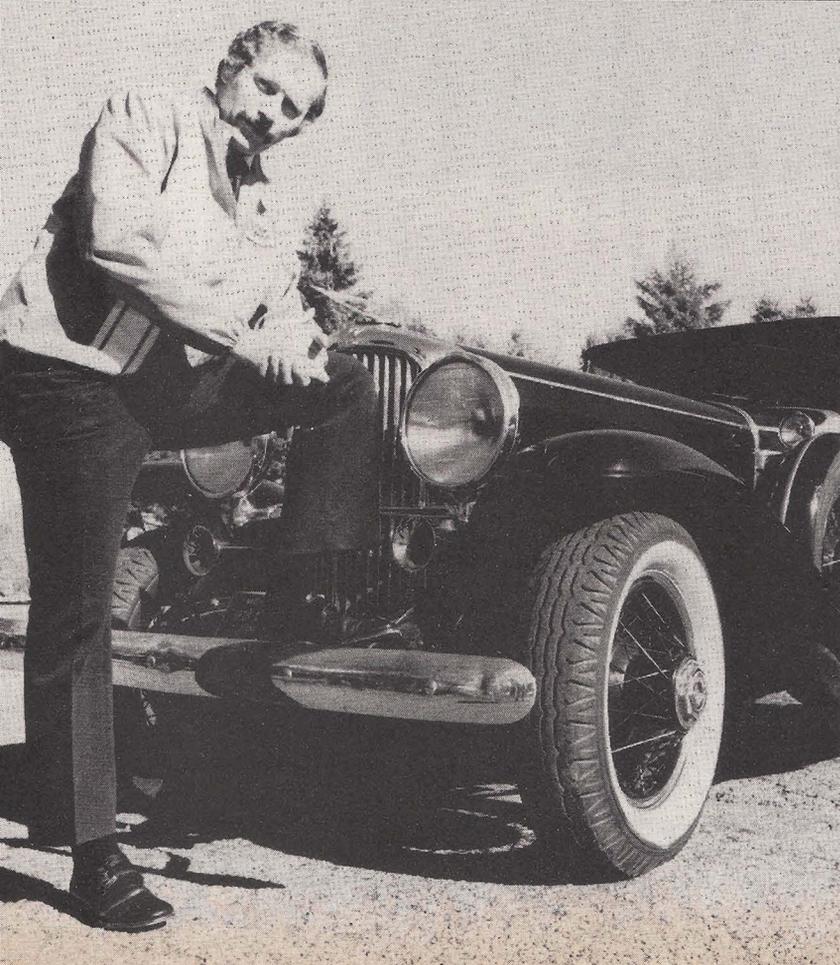
## You don't have to buy a new car to get an electronic ignition.



Most of you know the evaluation of automotive electrical systems . . . an evaluation characterized only occasionally by efficiency and performance. I know that, and that's why I use the Delta Mark Ten B CDI on all my cars, new and old. And believe me, you don't have to have a new car to appreciate the best electronic ignition available today. Study these features and you'll know what I mean.

1. Mark Ten and Mark Ten B Capacitive Discharge Ignition Systems are manufactured by Delta Products, Inc., a company with a conscience, and with a proven record of reliability both in product and in customer relations.
2. The Mark Ten CDI's really do save money by eliminating the need for 2 out of 3 tune-ups. Figure it out for yourself. The first tune-up or two saved pays for the unit, the rest is money in your pocket. No bunk!
3. Because the Mark Ten CDI's keep your car in better tune, you actually can save on expensive gasoline.
4. With a Mark Ten, spark plugs stay clean and last longer . . . fouling is virtually eliminated.



No matter what kind of car you drive, it too can use a Delta quality lift.

I want to know more about Mark Ten B CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



**DELTA PRODUCTS, INC.**

P.O. Box 1147, Dept. PE, Grand Junction, Colo. 81501  
303-242-9000

Mark Ten B,  
assembled . . . . . \$64.95 ppd  
Mark Ten B, kit . . . . . \$49.95 ppd

Standard Mark Ten,  
assembled . . . . . \$49.95 ppd  
Deltakit® . . . . . \$34.95 ppd